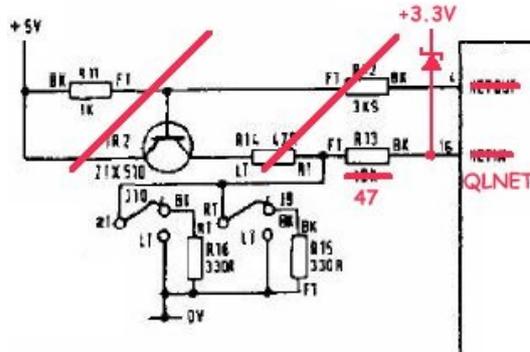



## QL Network on the Q68

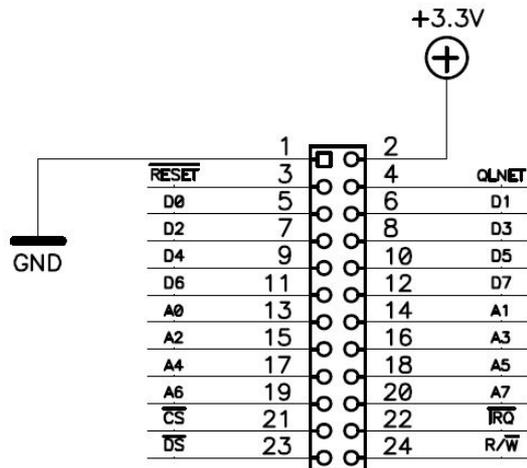Q68 network circuitry painted into the corresponding part of the original QL schematics:



Note: If the Q68 is only used as network endpoint, only a 3.5 mm jack without switch, one 47 Ω, one 330 Ω resistor and a schottky diode (e.g. BAT43) are needed.

Pinout of the Q68 Extension Bus (only QLNET, 3.3V and GND needed):



Position of Q68 Extension Bus on the Mainboard (green, Pin 1 marked):

